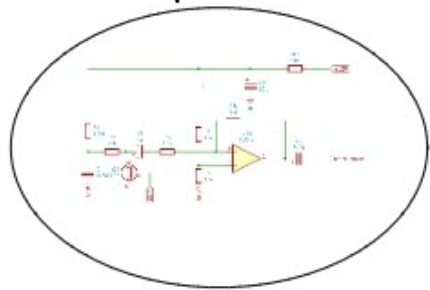


# Snare Drum


Based on Korg KR55

Voltage Controlled  
Amplifier (VCA)

- Feeds White Noise into signal



External White Noise Circuit

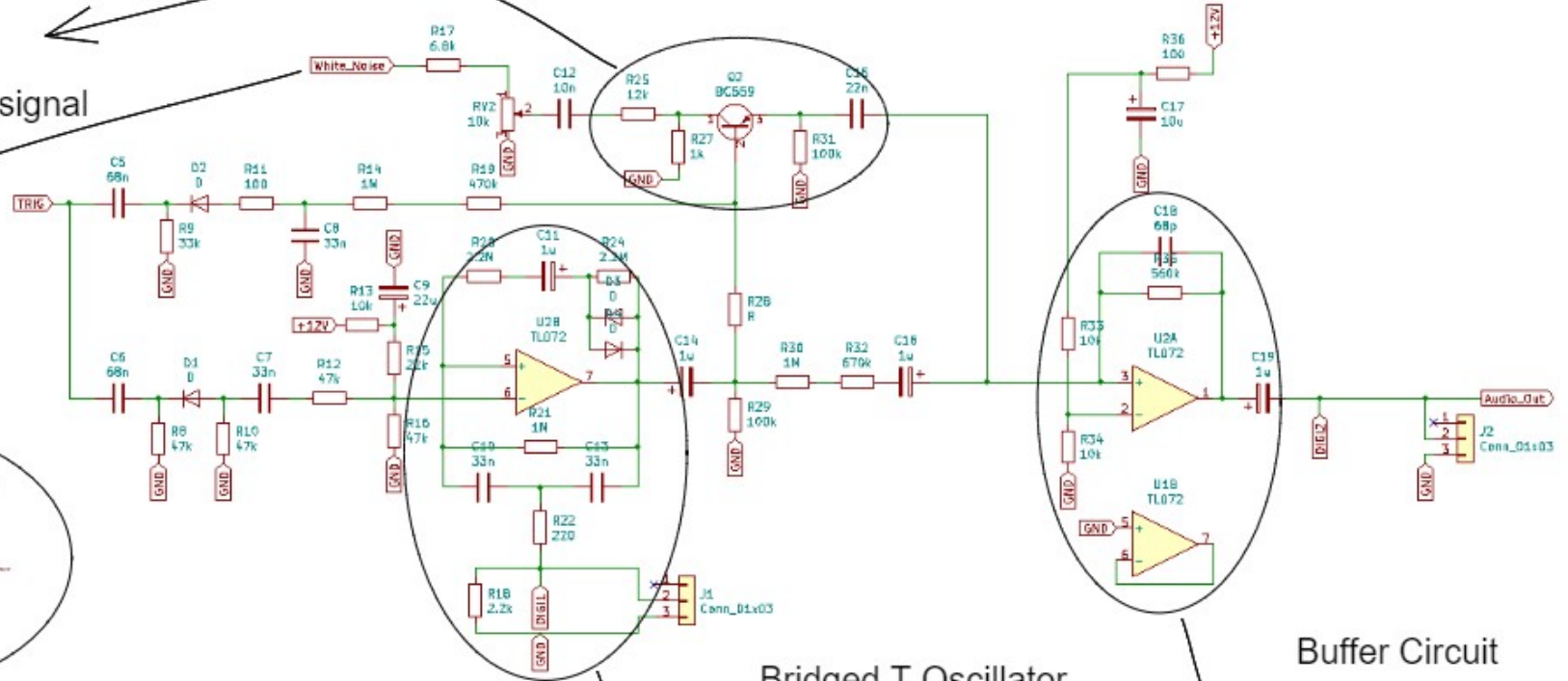

Bridged T Oscillator  
- Generates Envelope

Buffer Circuit

- Negative Trigger Required
- Largest Drum PCB Designed

- Can Adjust Frequency/Decay in Oscillator and Volume/Level at output of Buffer, and Noise Level in Noise Circuit