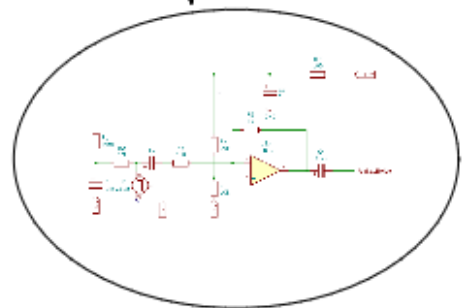


Snare Drum


Based on Korg KR55

Voltage Controlled
Amplifier (VCA)

- Feeds White Noise into signal



External White Noise Circuit

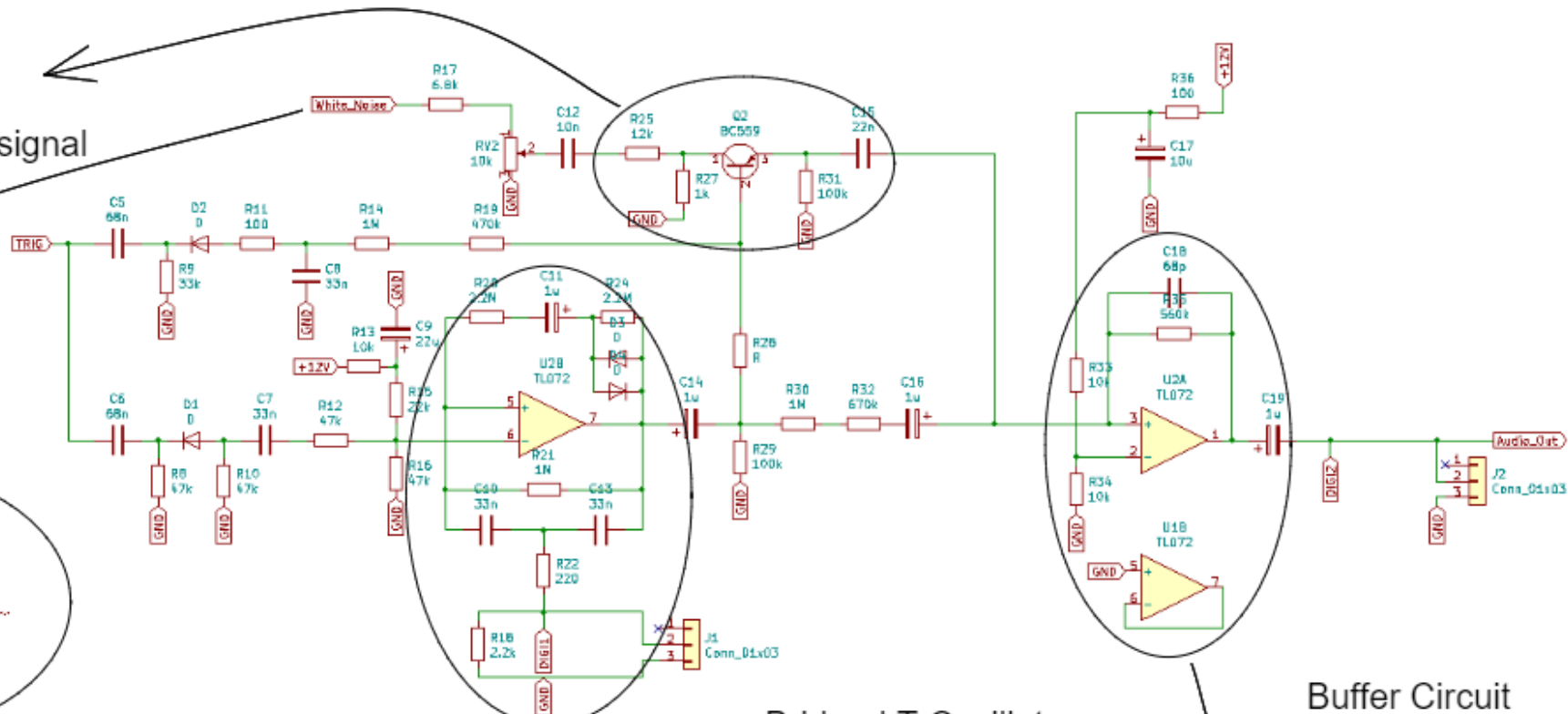

Bridged T Oscillator
- Generates Envelope

Buffer Circuit